

--	--	--	--	--	--	--	--	--	--

# MULTIMEDIA UNIVERSITY

## FINAL EXAMINATION

TRIMESTER 2, 2017/2018

### DET5068 – ANALOG ELECTRONICS 1

(Diploma in Electronic Engineering)

13 MARCH 2018  
2:30 PM – 4:30 PM  
(2 HOURS)

---

#### INSTRUCTIONS TO STUDENT

1. This question paper consists of 11 pages (5 pages with 5 questions and 6 pages for appendix).
2. Answer **ALL** questions. All necessary working steps must be shown.
3. Write all your answers in the answer booklet provided.

**QUESTION 1 [20 Marks]**

a) Materials on Earth can be classified into 3 broad categories which are conductor, semiconductor and insulator. Thus, define each of the terms, explain their electron valence characteristics and gives 2 examples for each of the material categories.

(6 marks)

b) Estimate the force of attraction,  $F_a \propto \frac{1}{d}$  and energy of electron,  $E \propto d$  relationship for electron,  $e_1$  and electron,  $e_2$  with calculation base on the information below. State which electron have the higher possibility of escaping the valence band into the conduction band.

(i) Electron,  $e_1$  has  $d_1 = 2 \times 10^{-20} m$  and electron,  $e_2$  has  $d_2 = 4 \times 10^{-20} m$

(7 marks)

(ii) Electron,  $e_1$  has  $d_1 = 3 \times 10^{-25} m$  and electron,  $e_2$  has  $d_2 = 5 \times 10^{-25} m$

(7 marks)

Continued...

**QUESTION 2 [20 Marks]**

a)

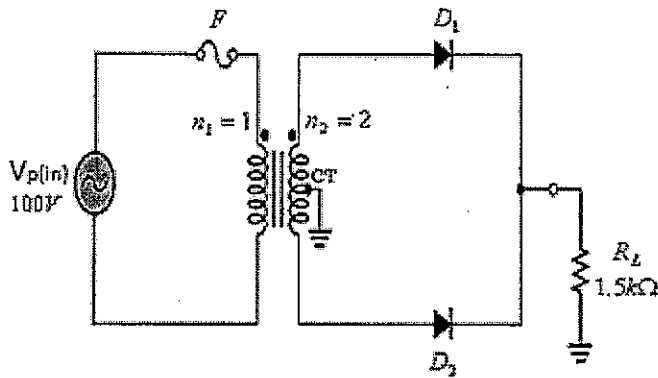


Figure 1(a)

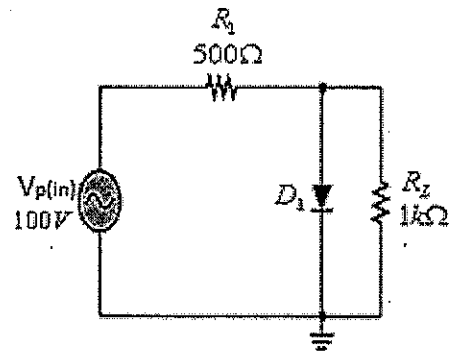


Figure 1(b)

Figure 1(a) and Figure 1(b) shows 2 types of diode application. Calculate the output voltage for each of the application using the given values.

(10 marks)

b) Draw the voltage-current characteristic curve of a normal diode and a Zener diode. Compare and state the difference between both voltage-current characteristic curve.

(10 marks)

Continued...

**QUESTION 3 [20 Marks]**

(a) A certain BJT has base current,  $I_B = 50\mu A$  and collector current,  $I_C = 5.66mA$ . Determine the following:

- (i) DC beta,  $\beta_{DC}$
- (ii) emitter current,  $I_E$
- (iii) DC alpha,  $\alpha_{DC}$

(6 marks)

(b)

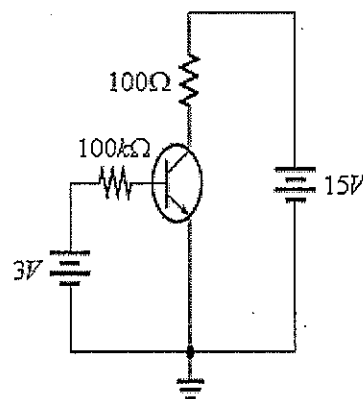


Figure 2

Figure 2 shows a transistor circuit bias. Determine the followings, if  $\beta_{DC} = 200$ .

- (i)  $I_B$  (5 marks)
- (ii)  $I_C$  (1 mark)
- (iii)  $I_E$  (3 marks)
- (iv)  $V_{CE}$  (2 marks)
- (v)  $V_{BE}$  (1 mark)
- (vi)  $V_{CB}$  (2 marks)

Continued...

**QUESTION 4 [20 Marks]**

An emitter bias circuit for BJT is having the following parameters:  $R_C = 4.2k\Omega$ ,  $R_B = 55k\Omega$ ,  $R_E = 9.5k\Omega$ ,  $V_{CC} = 20V$ ,  $V_{EE} = -20V$  and  $\beta_{DC} = 130$ . Based on the information given:

(a) Sketch the circuit diagram

(5 marks)

(b) Evaluate the Q-point of the circuit.

(15 marks)

Continued...

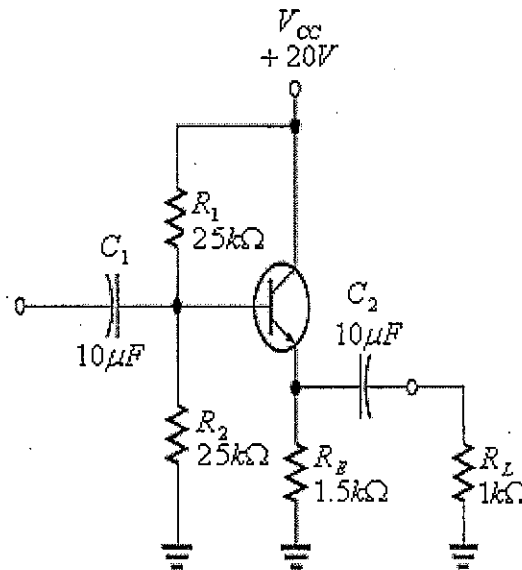
**QUESTION 5 [20 Marks]**

Figure 3

Figure 3 shows a certain type of BJT amplifier. Given that  $\beta_{ac} = 90$  and  $V_{in} = 1.5mV_{rms}$ .

(a) Identify the amplifier

(1 mark)

(b) Calculate  $R_{in(tot)}$

(7 marks)

(c) Calculate  $A_v$

(1 mark)

(d) Calculate  $A_i$

(10 marks)

(e) Calculate  $A_p$

(1 mark)

**End of Page.**

### FORMULAE LIST

BJT BIAS	
TERMS	FORMULAE
DC load line equation	$I_C = -\frac{1}{R_C}V_{CE} + \frac{V_{CC}}{R_C}$
<b>Voltage divider-bias:</b>	
DC collector and emitter current	$I_C \cong I_E = \frac{V_E}{R_E}$
DC base voltage	$V_B = \frac{R_2 // R_{IN(BASE)}}{R_1 + (R_2 // R_{IN(BASE)})} \times V_{CC}$ $V_B = \frac{R_2}{R_1 + R_2} \times V_{CC} \quad \text{if, } R_{IN(BASE)} \gg R_2$
DC collector voltage	$V_C = V_{CC} - I_C R_C$
DC collector-to-emitter voltage	$V_{CE} = V_{CC} - I_C (R_C + R_E)$
DC emitter voltage	$V_E = V_B - V_{BE}$
DC input resistance at the base	$R_{IN(BASE)} = \beta_{DC} R_E$
DC total resistance	$R_T = R_2 // \beta_{DC} R_E$
<b>Base bias:</b>	
DC base current	$I_B = \frac{V_{CC} - V_{BE}}{R_B}$

DC collector current	$I_C = \frac{\beta_{DC}(V_{CC} - V_{BE})}{R_B}$
DC collector-to-emitter voltage	$V_{CE} = V_{CC} - I_C R_C$
<b>Collector-feedback bias:</b>	
DC base current	$I_B = \frac{V_C - V_{BE}}{R_B}$
DC collector current	$I_C = \frac{V_{CC} - V_{BE}}{\frac{R_B}{\beta_{DC}} + R_C}$
DC collector-to-emitter voltage	$V_{CE} = V_{CC} - I_C R_C$
<b>Emitter bias:</b>	
DC base current	$I_B \cong \frac{I_E}{\beta_{DC}}$
DC collector current	$I_C \cong \frac{-V_{EE} - V_{BE}}{\frac{R_B}{\beta_{DC}} + R_E}$
DC emitter current	$I_E = \frac{-V_{EE} - V_{BE}}{\frac{R_B}{\beta_{DC}} + R_E}$
DC base voltage	$V_B = V_E + V_{BE}$
DC collector voltage	$V_C = V_{CC} - I_C R_C$
DC collector-to-emitter voltage	$V_{CE} = V_C - V_E$



DC emitter voltage	$V_E = V_{EE} + I_E R_E$
<b>BJT AMPLIFIERS</b>	
TERMS	FORMULAE
<b>r Parameters:</b>	
ac base resistance	$r_b' = h_{ie} - \frac{h_{re}(h_{fe} + 1)}{h_{oe}}$
ac collector resistance	$r_c' = \frac{h_{re} + 1}{h_{oe}}$
ac emitter resistance	$r_e' = \frac{h_{re}}{h_{oe}}$
<b>Common-base amplifier:</b>	
DC emitter current	$I_E = \frac{V_E}{R_E}$
DC base voltage	$V_B = \frac{R_2}{R_1 + R_2} \times V_{CC}$
DC emitter voltage	$V_E = V_B - V_{BE}$
ac output voltage	$V_{out} = V_c$
ac input voltage	$V_{in} = V_e$
ac resistance at emitter	$R_{in(emitter)} \cong r_e'$
ac output resistance	$R_{out} \cong R_C$

Current gain	$A_i \cong 1$
Voltage gain	$A_v \cong \frac{R_c}{r_e}$
Power gain	$A_p = A_v$
<b>Common-collector amplifier:</b>	
ac input current	$I_{in} = \frac{V_{in}}{R_{in(tot)}}$
ac emitter current	$I_e = \frac{V_e}{R_e}$
ac emitter voltage	$V_e = A_v V_b$
ac input resistance at base	$R_{in(base)} \cong \beta_{ac} R_e$
ac total input resistance	$R_{in(tot)} = R_1 // R_2 // R_{in(base)}$
ac output resistance	$R_{out} \cong \left( \frac{R_s}{\beta_{ac}} \right) // R_E$
Current gain	$A_i = \frac{I_e}{I_{in}}$
Voltage gain	$A_v \cong 1$
Power gain	$A_p = A_i$

<b>Common-emitter amplifier:</b>	
DC collector current	$I_C \cong I_E$
DC base voltage	$V_B = \frac{R_2}{R_1 + R_2} \times V_{CC}$
DC collector voltage	$V_C = V_{CC} - I_C R_C$
DC collector-to-emitter voltage	$V_{CE} = V_C - V_E$
DC emitter current	$I_E = \frac{V_E}{R_E}$
DC emitter voltage	$V_E = V_B - V_{BE}$
DC input resistance at base	$R_{IN(BASE)} = \beta_{DC} R_E$
ac base current	$I_b \cong \frac{I_e}{\beta_{ac}}$
ac base voltage	$V_b = \frac{R_{in(tot)}}{R_s + R_{in(tot)}} \times V_s$ $= I_e' r_e'$
ac collector voltage	$V_c = A_v' V_x$
ac total current signal	$I_s = \frac{V_s}{R_{in(tot)} + R_s}$

ac input resistance at base	$R_{in(base)} = \beta_{ac} r'_e$
ac total input resistance	$R_{in(tot)} = R_1 // R_2 // R_{in(base)}$
ac output resistance	$R_{out} \cong R_C$
Current gain	$A_i = \frac{I_c}{I_s}$
Voltage gain	$A_v = \frac{R_C}{r'_e}$ if $C_2$ exists $A_v = \frac{R_C}{r'_e + R_E}$ if $C_2$ does not exist
Overall voltage gain	$A'_v = Attenuation \times A_v$
Power gain	$A_p = A'_v A_i$